

1. Truth Table for the 2-bit Arithmetic and Logic Units

Inputs				Equal	Greater	Less	Arithmetic		Output
A1	A0	B1	B0	Magnitude(E)	A > B	A < B	Operation		
0	0	0	0	1	0	0	Multiply		00
0	0	0	1	0	0	1	Add		01
0	0	1	0	0	0	1	Add		10
0	0	1	1	0	0	1	Add		11
0	1	0	0	0	1	0	Subtract		01
0	1	0	1	1	0	0	Multiply		00
0	1	1	0	0	0	1	Add		11
0	1	1	1	0	0	1	Add		10
1	0	0	0	0	1	0	Subtract		01
1	0	0	1	0	1	0	Subtract		10
1	0	1	0	1	0	0	Multiply		10
1	0	1	1	0	0	1	Add		01
1	1	0	0	0	1	0	Subtract		11
1	1	0	1	0	1	0	Subtract		10
1	1	1	0	0	1	0	Subtract		01
1	1	1	1	1	0	0	Multiply		11

From the above truth table logical expressions for each output can be expressed as follows:

$$A = B : A1'A0'B1'B0' + A1'A0B1'B0 + A1A0B1B0 + A1A0'B1B0'$$

$$: A1'B1' (A0'B0' + A0B0) + A1B1 (A0B0 + A0'B0')$$

$$: (A0B0 + A0'B0') (A1B1 + A1'B1')$$

$$: (A0 \text{ Ex-Nor } B0) (A1 \text{ Ex-Nor } B1)$$

$$A < B : A1'B1 + A0'B1B0 + A1'A0'B0$$

$$A > B : A1B1' + A0B1'B0' + A1A0B0'$$

Selected Output Solution

Input 1: (A=00, B=00)

multiply:

$$00 \times 00 = 00 \quad \text{output} = 00$$

Input 2: (A=00, B=01)

Arithmetic operation: Add

$$\begin{array}{r} 00 \\ + 01 \\ \hline 01 \end{array}$$

$$\text{output} = 01$$

Input 3: (A=00, B=10)

Arithmetic operation: Add

$$\begin{array}{r} 00 \\ + 10 \\ \hline 10 \end{array}$$

$$\text{Output} = 10$$

Input 4: (A=00, B=11)

Arithmetic operation: Add

$$\begin{array}{r} 00 \\ + 11 \\ \hline 11 \end{array}$$

$$\text{output} = 11$$

Input 5: (A=01, B=00)

Subtract:

$$\begin{array}{r} 01 \\ - 00 \\ \hline 01 \end{array}$$

$$\text{output} = 01$$

Input 6: (A=01, B=01)

multiply $01 \times 01 = 01$

Multiplexer selection:

The control signals dictate which output is chosen

Since $F=1$ (both A and B are equal)
the multiplexers select the output of
the multiplier
where $F1=0$ and $F0=0$ output=00


Input 7: 01

Add

$$\begin{array}{r} 10 \\ 11 \\ \hline \end{array}$$

$$\text{output} = 11$$

Logic circuit diagram

 

2. A Finite State Machine has an ending input, it is made up of two types, that's finite state machine with output and finite state machine without output. In the given question finite state machine without output can be used. (Deterministic Finite State Automata).

Diagram's explanation
from the question,
 $\Sigma = \{0, 1\}$ (input alphabet) $Q =$ Set of all states $\{A, B, C, D, E\}$
 $F = \{E\}$ (final state)
Starting from A, we move to state B when the input was 0, it
attains the state A whenever the output is 1.
State B also attains an output of 1 and sends it back to state
A. It moves to C with an input of 0, where state C also moves
to state D whenever the output is 1, and finally state D passes on to
state E (final state) which gives out the required answer that it
ends with 1 (final state) it ends with 2 consecutive 1, 1, 1
has four length string thus $\{0011, 0111, 1011, \dots\}$

26. Transition table for the finite state machine.

States	0	1
A	B	A
B	C	A
C	C	D
D	B	E
E	E	E

Explanation: When either of the
state attains an input
 $\Sigma = \{0, 1\}$ where does it go,
does it stay in the same state
or it moves to another state.

b. **JK flip flop:** The JK flip flop is just like the **SR Flip flop** but there are some slide changes in the JK's. with Jk flip flop there is no change in the state when both J and K are **low**. To get better understanding of the JK flip flop there is a need to know everything about the NAND gate, especially their truth table.

NAND Gate Truth Table

A	B	C	AND Output	NAND
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

Explanation: NAND Gate is the complement of the AND Gate, where 0 changes to 1 and 1 changes to 0

with the help of the **NAND** gate, we can derive characteristics table, k-map and the excitation table for JK flip flop.

Characteristics Table for JK flip flop.

J	K	Q_n	Q_{n+1}	
x	x	0/1	0/1	Q_n
0	0	0	0	Q_n
0	0	1	1	
0	1	0	0	Reset (0)
0	1	1	0	
1	0	0	1	Set(1)
1	0	1	1	
1	1	0	1	Q_n' Toggle
1	1	1	0	

Explanation:


a. When J and K are zero(Q_n) the flip flop will return its current state.

b. When J is 0 and K is 1, irrespective of the previous state the current state will be 0 for both.

c. Also, when j is 1 and k is 0 the current state will be 1, irrespective of the previous state.

 d. When both J and K are 1 there would be a toggle where 1 will have a complement of 0 and too will have a complement of 1.

From the table we can draw a k-map to simplify the expression. From the table the minterms(m2, m3, m4 and m6) had an output of 1 each in the current state(Q_{n+1}), therefore we draw a k-map to simplify the given expression.



JK flip flop Excitation Table

Q_n	Q_{n+1}	J	K	Description from characteristic table
0	0	0	x	In Q_n and reset column J is not changing but K is changing.
0	1	1	X	From set and toggle column j is not changing but k is changing, so we assign it to x
1	0	x	1	From reset and toggle column j is changing but k remains 1.
1	1	x	0	Toggle happens here, meaning we complement Q_n for toggle state.

Circuit diagram for the JK flip flop

